LAB SHEET 2

MEASURE THE RISE TIME OF THE RC CIRCUIT FOR THREE VALUES OF THE RESISTOR.

1. R IS 1 K, C IS 10 N.
2. R IS 2 K, C IS 10 N.
3. R IS 5 K, C IS 10 N.

PLOT THE TIME AGAINST R.

LAB SHEET 2

MEASURE THE RISE TIME OF THE RC CIRCUIT FOR THREE VALUES OF THE RESISTOR.

1. R IS 1 K, C IS 10 N.
2. R IS 2 K, C IS 10 N.
3. R IS 5 K, C IS 10 N.

PLOT THE TIME AGAINST R.